

Accelerator Physics

Particle Acceleration


G. A. Krafft

Old Dominion University

Jefferson Lab

Lecture 3

Transmission Lines

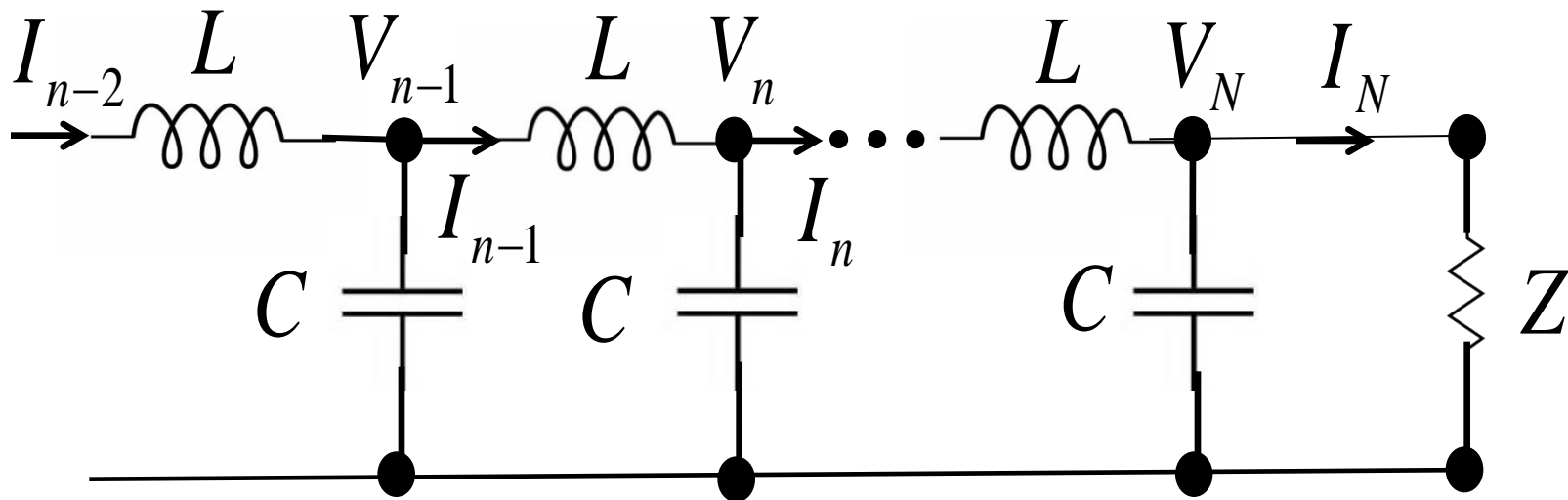

Inductor Impedance and Current Conservation

$$V_{n-1} - V_n = i\omega L I_{n-1}$$

$$I_{n-1} - I_n = i\omega C V_n$$

Transmission Line Equations



- Standard Difference Equation with Solution

$$V_n = V_0 e^{-in\lambda}, I_n = I_0 e^{-in\lambda}$$

$$V_0 (e^{i\lambda} - 1) = i\omega L I_0 e^{i\lambda} \quad I_0 (e^{i\lambda} - 1) = i\omega C V_0$$

$$2\sin(\lambda/2) = \pm\omega\sqrt{LC}$$

$$V^+ = \sqrt{L/C} I^+ e^{i\lambda/2} \quad V^- = -\sqrt{L/C} I^- e^{i\lambda/2}$$

- Continuous Limit ($N \rightarrow \infty$)


$$\lambda \rightarrow \pm\omega\sqrt{LC} \quad k = \omega\sqrt{L'C'} \quad v_\phi = 1/\sqrt{L'C'}$$

$$V^+(x, t) = V_0^+ e^{i\omega t - kx} = \sqrt{L'/C'} I_0^+ e^{i\omega t - kx} = Z_0 I_0^+ e^{i\omega t - kx}$$

$$V^-(x, t) = V_0^- e^{i\omega t + kx} = -\sqrt{L'/C'} I_0^- e^{i\omega t + kx} = -Z_0 I_0^- e^{i\omega t + kx}$$

Cavity Coupled to an RF Source

- Equivalent Circuit

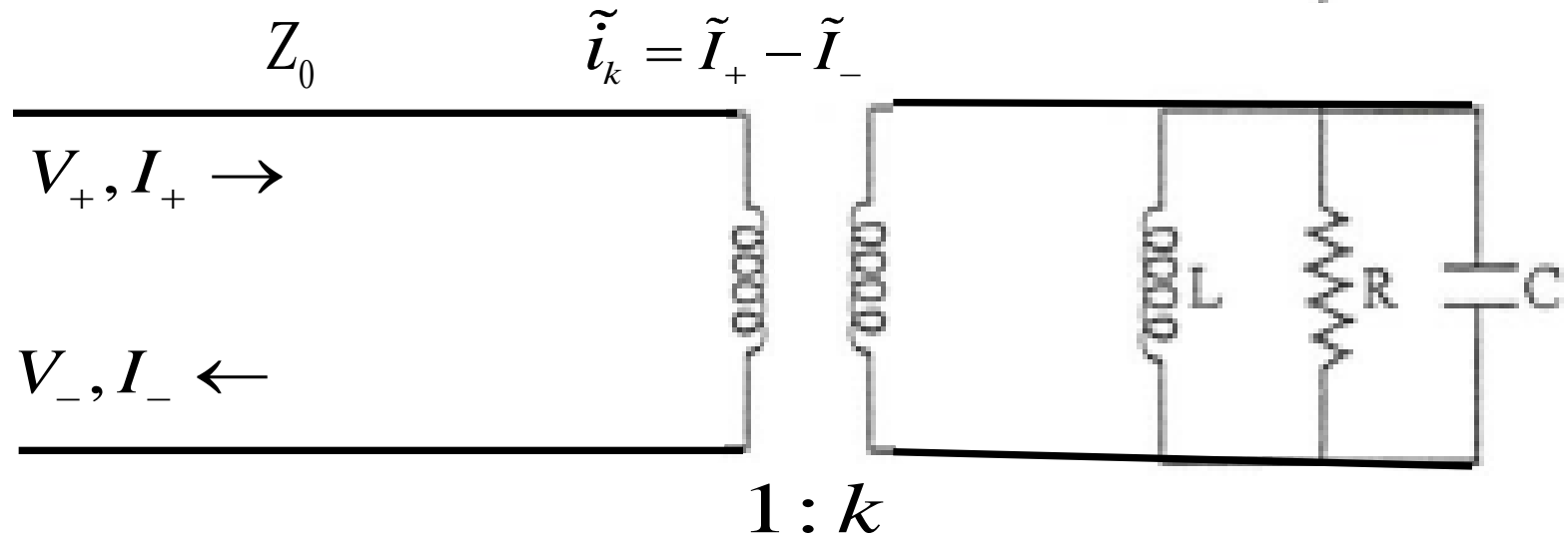

RF Generator + Circulator

Coupler

Cavity

- Coupling is represented by an ideal (lossless) transformer of turns ratio $1:k$

Cavity Coupled to an RF Source



- From transmission line equations, forward power from RF source

$$|V_+|^2 / 2Z_0$$

- Reflected power to circulator

$$|V_-|^2 / 2Z_0$$

- Transformer relations

$$V_c = kV_k = k(V_+ + V_-)$$

$$i_c = i_k / k = (I_+ - I_-) / k = 2I_+ / k - V_c / (k^2 Z_0)$$

- Considering zero forward power case and definition of β


$$\beta = (|V_-|^2 / 2Z_0) / (|V_c|^2 / 2R) = R / (k^2 Z_0)$$

Cavity Coupled to an RF Source

- Loaded cavity looks like

$$i_g(t) = \frac{2I_+(t)}{k}$$
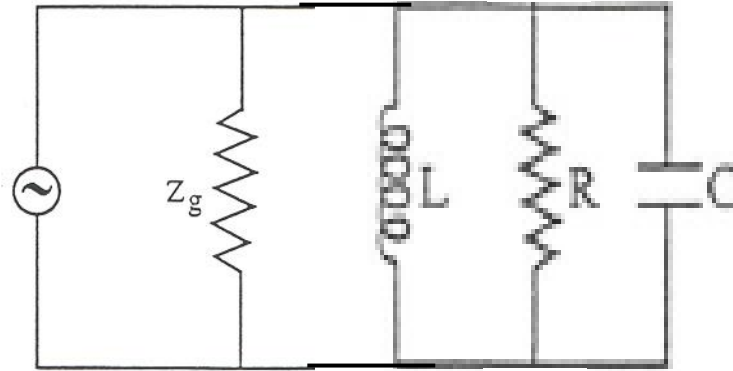
$$= \text{Re}\left(\tilde{i}_g e^{i\omega t}\right)$$



$$\beta \equiv \frac{R}{Z_g} = \frac{R}{k^2 Z_0} \quad \therefore \quad Z_g = \frac{R}{\beta}$$

Wiedemann
Fig. 16.1

Wiedemann
16.1

- Effective and loaded resistance

$$\frac{1}{R_{eff}} = \frac{1}{R} + \frac{1}{Z_g} = \frac{1+\beta}{R} \quad R_L = 2R_{eff} = \frac{R_a}{1+\beta}$$

- Solving transmission line equations

$$V_+ = \frac{1}{2} \left(\frac{V_c}{k} + kZ_0 i_c \right) \quad V_- = \frac{1}{2} \left(\frac{V_c}{k} - kZ_0 i_c \right)$$

Powers Calculated



- Forward Power

$$P_g = \frac{V_c^2}{8Z_0 k^2} \left| 1 + \frac{1}{\beta} \left[1 + iQ_0 \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right) \right] \right|^2 = \frac{V_c^2}{R_a} \frac{(1+\beta)^2}{4\beta} \left(1 + Q_L^2 \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right)^2 \right)$$

- Reflected Power

$$P_{refl} = \frac{V_c^2}{8Z_0 k^2} \left| 1 - \frac{1}{\beta} \left[1 + iQ_0 \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right) \right] \right|^2 = \frac{V_c^2}{R_a} \frac{(1+\beta)^2}{4\beta} \left(\frac{(\beta-1)^2}{(1+\beta)^2} + Q_L^2 \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right)^2 \right)$$

- Power delivered to cavity is

$$P_g - P_{refl} = \frac{V_c^2}{R_a} \frac{(1+\beta)^2}{4\beta} \left[1 - \frac{(\beta-1)^2}{(1+\beta)^2} \right] = \frac{V_c^2}{R_a} = P_{diss}$$

as it must by energy conservation!

Some Useful Expressions

- Total energy W , in terms of cavity parameters

$$\frac{W}{P_g} = \frac{Q_0 P_{diss}}{\omega_0 P_{diss}} \frac{4\beta}{(1+\beta)^2} \frac{1}{1 + Q_L^2 \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right)^2}$$

$$\therefore W = 4\beta \frac{Q_0}{\omega_0} \frac{1}{(1+\beta)^2 + Q_0^2 \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right)^2} P_g$$

$$\omega \approx \omega_0 \Rightarrow W \approx \frac{4\beta}{(1+\beta)^2} \frac{Q_0}{\omega_0} \frac{1}{1 + \left[2Q_L \frac{\omega - \omega_0}{\omega_0} \right]^2} P_g$$

- Total impedance

$$Z_{TOT} = \left[\frac{1}{Z_g} + \frac{1}{Z} \right]^{-1}$$

$$Z_{TOT} = \frac{R_a}{2} \left[(1+\beta) + iQ_0 \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right) \right]^{-1}$$

When Cavity is Detuned



- Define “Tuning angle” Ψ :

$$\tan \Psi \equiv -Q_L \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right) \approx -2Q_L \frac{\omega - \omega_0}{\omega_0} \quad \text{for } \omega \approx \omega_0$$

\therefore

$$W = \frac{4\beta}{(1+\beta)^2} \frac{Q_0}{\omega_0} \frac{1}{1+\tan^2 \Psi} P_g$$

Wiedemann
16.12

- Note that:

$$P_{diss} = \frac{4\beta}{(1+\beta)^2} \frac{1}{1+\tan^2 \Psi} P_g$$

Optimal β Without Beam

- Optimal coupling: W/P_g maximum or $P_{diss} = P_g$
which implies for $\Delta\omega = 0$, $\beta = 1$

This is the case called “critical” coupling

- Reflected power is consistent with energy conservation:

$$P_{refl} = P_g - P_{diss}$$


$$P_{refl} = P_g \left[1 - \frac{4\beta}{(1+\beta)^2} \frac{1}{1+\tan^2 \Psi} \right]$$

- On resonance:

$$W = \frac{4\beta}{(1+\beta)^2} \frac{Q_0}{\omega_0} P_g$$


$$P_{diss} = \frac{4\beta}{(1+\beta)^2} P_g$$
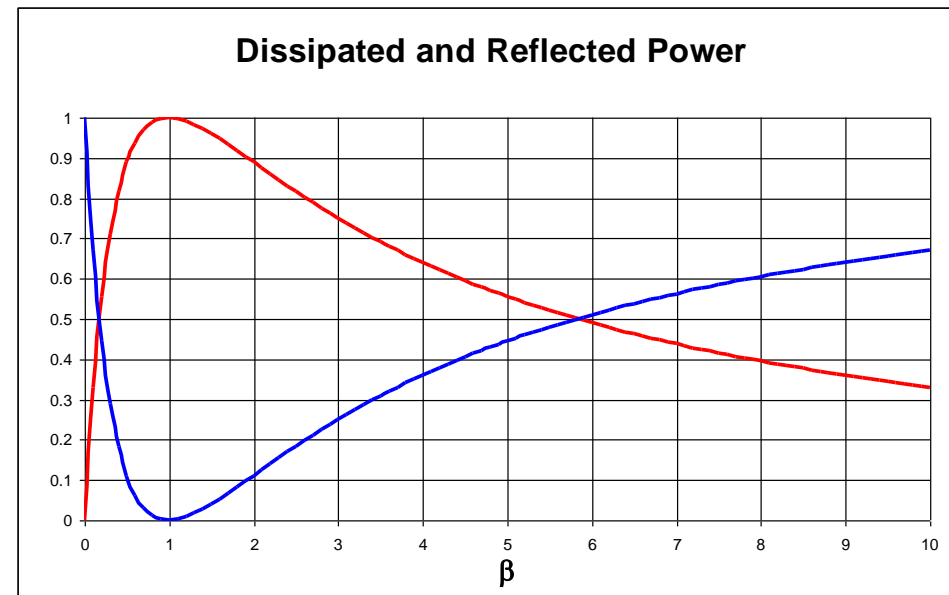
$$P_{refl} = \left(\frac{1-\beta}{1+\beta} \right)^2 P_g$$



Equivalent Circuit: Cavity with Beam

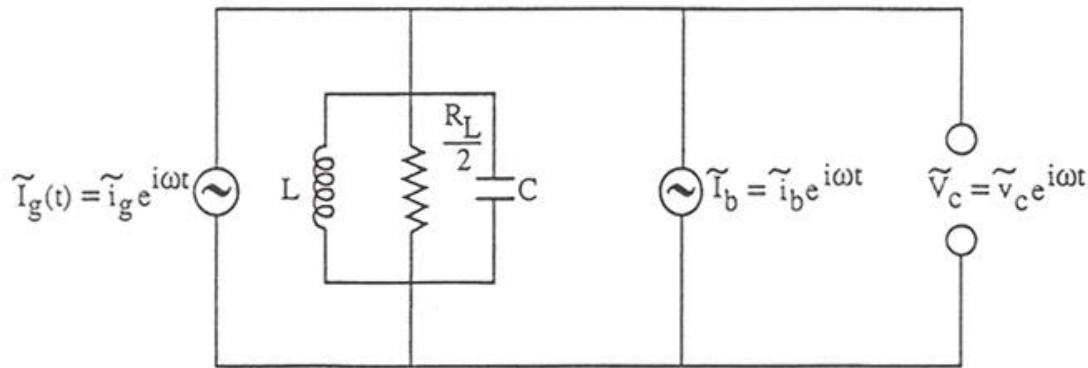- Beam through the RF cavity is represented by a current generator that interacts with the total impedance (including circulator).
- Equivalent circuit:



$$i_c = C \frac{dV_c}{dt}, \quad i_R = \frac{V_c}{R_L / 2}, \quad V_c = L \frac{di_L}{dt}$$

i_g the current induced by generator, i_b beam current

- Differential equation that describes the dynamics of the system:

$$\frac{d^2 V_c}{dt^2} + \frac{\omega_0}{Q_L} \frac{dV_c}{dt} + \omega_0^2 V_c = \frac{\omega_0 R_L}{2Q_L} \frac{d}{dt} (i_g - i_b)$$

Cavity with Beam



- Kirchoff's law:

$$i_L + i_R + i_C = i_g - i_b$$

- Total current is a superposition of generator current and beam current and beam current opposes the generator current.
- Assume that voltages and currents are represented by complex phasors

$$V_c(t) = \text{Re}(\tilde{V}_c e^{i\omega t})$$

$$i_g(t) = \text{Re}(\tilde{i}_g e^{i\omega t})$$

$$i_b(t) = \text{Re}(\tilde{i}_b e^{i\omega t})$$

where ω is the generator angular frequency and $\tilde{V}_c, \tilde{i}_g, \tilde{i}_b$ are complex quantities.

Voltage for a Cavity with Beam



- Steady state solution

$$(1 - i \tan \Psi) \tilde{V}_c = \frac{R_L}{2} (\tilde{i}_g - \tilde{i}_b)$$

where Ψ is the tuning angle.

- Generator current

$$|\tilde{i}_g| = 2I^+ = \frac{2}{k} \sqrt{\frac{2P_g}{Z_0}} = 2\sqrt{\beta} \sqrt{\frac{2P_g}{R}} = 4\sqrt{\beta} \sqrt{\frac{P_g}{R_a}}$$

- For short bunches: $|\tilde{i}_b| \approx 2I_0$ where I_0 is the average beam current.

Wiedemann 16.19

Voltage for a Cavity with Beam

- At steady-state:
$$\tilde{V}_c = \frac{R_L / 2}{(1 - i \tan \Psi)} \tilde{i}_g - \frac{R_L / 2}{(1 - i \tan \Psi)} \tilde{i}_b$$
- or
$$\tilde{V}_c = \frac{R_L}{2} \tilde{i}_g \cos \Psi e^{i\Psi} - \frac{R_L}{2} \tilde{i}_b \cos \Psi e^{i\Psi}$$
- or
$$\tilde{V}_c = \boxed{\tilde{V}_{gr} \cos \Psi e^{i\Psi}} + \boxed{\tilde{V}_{br} \cos \Psi e^{i\Psi}}$$
- or
$$\tilde{V}_c = \tilde{V}_g + \tilde{V}_b$$

$$\left\{ \begin{array}{l} \tilde{V}_{gr} = \frac{R_L}{2} \tilde{i}_g \\ \tilde{V}_{br} = -\frac{R_L}{2} \tilde{i}_b \end{array} \right\} \text{ are the generator and beam-loading} \\ \text{voltages on resonance}$$

and $\left\{ \begin{array}{l} \tilde{V}_g \\ \tilde{V}_b \end{array} \right\}$ are the generator and beam-loading voltages.

Voltage for a Cavity with Beam

- Note that:


$$|\tilde{V}_{gr}| = \frac{2\sqrt{\beta}}{\sqrt{1+\beta}} \sqrt{P_g R_L} \approx 2\sqrt{P_g R_L} \quad \text{for large } \beta$$

Wiedemann
16.16

$$|\tilde{V}_{br}| = R_L I_0$$


Wiedemann
16.20

Voltage for a Cavity with Beam

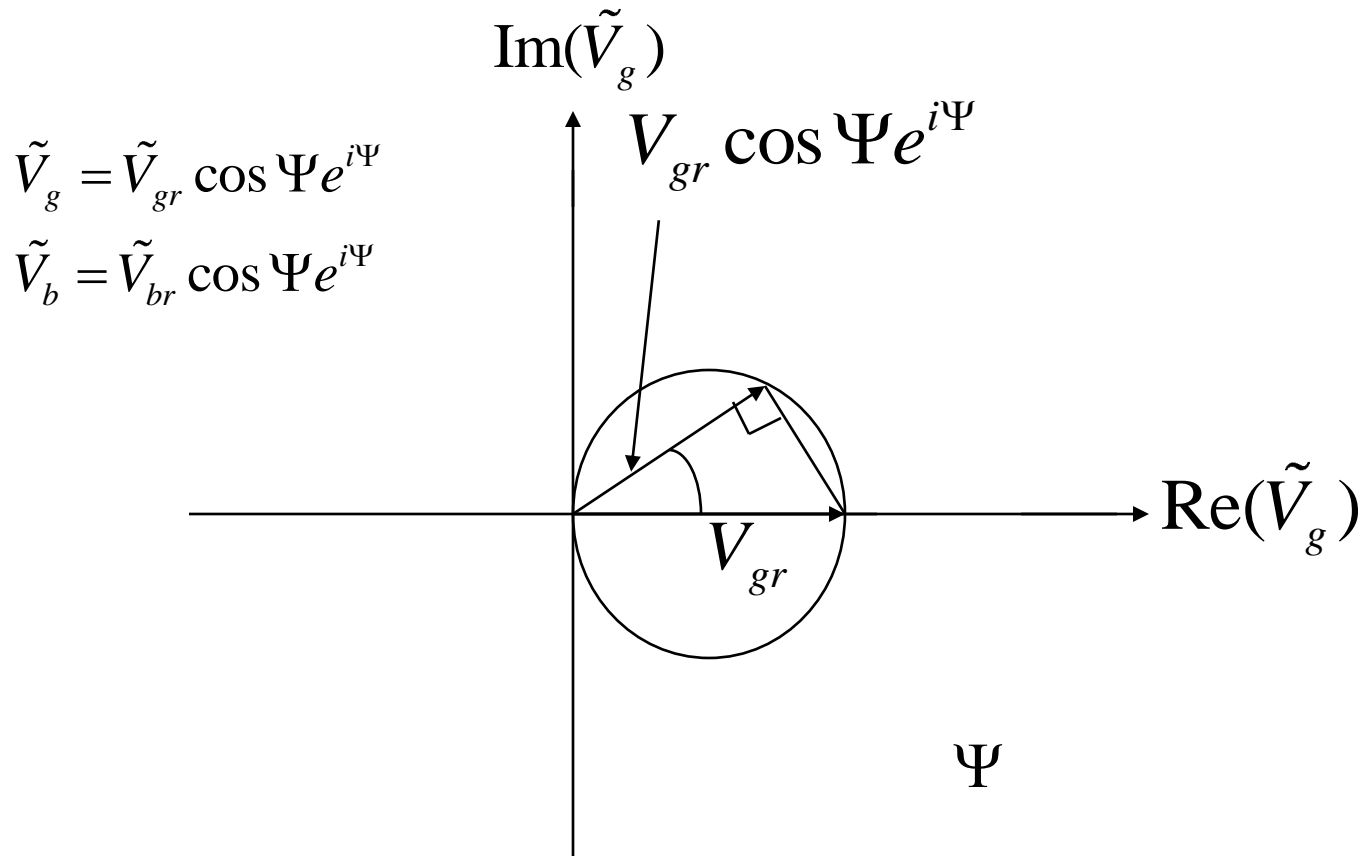

As Ψ increases, the magnitudes of both V_g and V_b decrease while their phases rotate by Ψ .


Example of a Phasor Diagram

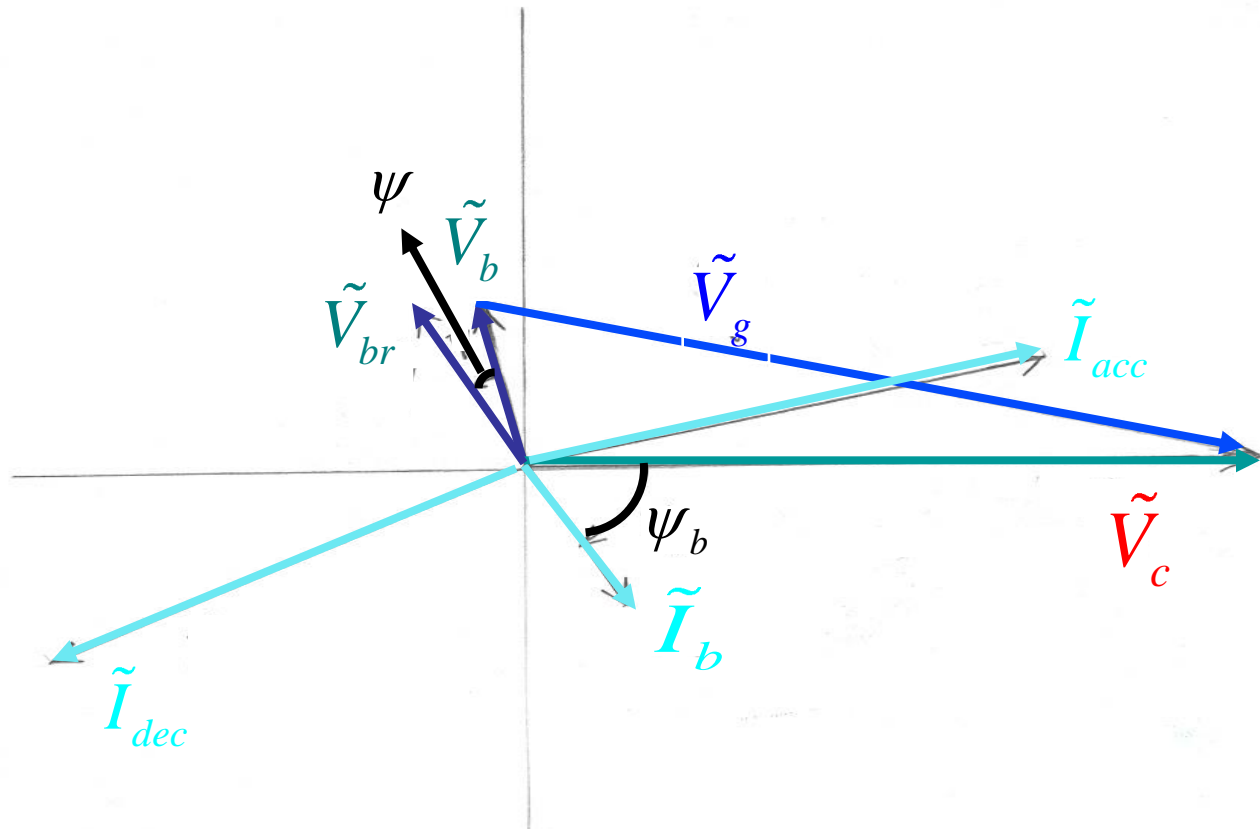

Wiedemann
Fig. 16.3

On Crest/On Resonance Operation

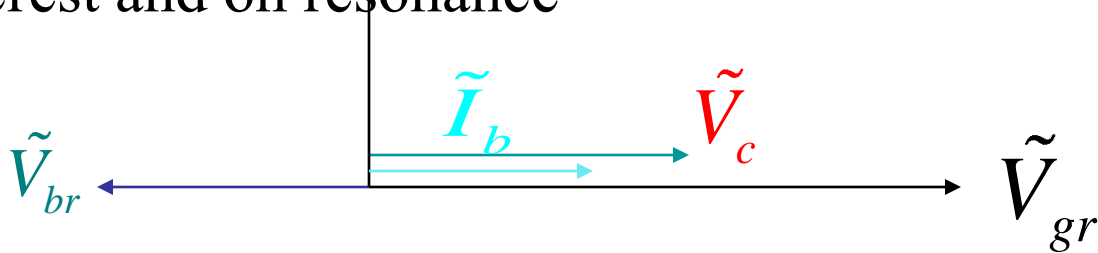- Typically linacs operate on resonance and on crest in order to receive maximum acceleration.
- On crest and on resonance



$$\Rightarrow V_c = V_{gr} - V_{br}$$

where V_c is the accelerating voltage.

More Useful Equations

- We derive expressions for W , V_a , P_{diss} , P_{refl} in terms of β and the loading parameter K , defined by: $K = I_0 \sqrt{R_a} / (2 \sqrt{P_g})$

$$V_c = \sqrt{P_g R_L} \left\{ \frac{2\sqrt{\beta}}{\sqrt{1+\beta}} \left(1 - \frac{K}{\sqrt{\beta}} \right) \right\}$$

From:

$$|\tilde{V}_{gr}| = \frac{2\sqrt{\beta}}{\sqrt{1+\beta}} \sqrt{P_g R_L}$$

$$|\tilde{V}_{br}| = R_L I_0$$

$$V_c = V_{gr} - V_{br}$$

$$W = \frac{4\beta}{(1+\beta)^2} \frac{Q_0}{\omega_0} \left(1 - \frac{K}{\sqrt{\beta}} \right)^2 P_g$$

$$P_{diss} = \frac{4\beta}{(1+\beta)^2} \left(1 - \frac{K}{\sqrt{\beta}} \right)^2 P_g$$

\Rightarrow

$$I_0 V_a = I_0 \sqrt{R_a P_{diss}}$$

$$\eta \equiv \frac{I_0 V_c}{P_g} = \frac{2\sqrt{\beta}}{\sqrt{1+\beta}} 2K \left(1 - \frac{K}{\sqrt{\beta}} \right)$$

$$P_{refl} = P_g - P_{diss} - I_0 V_a \Rightarrow P_{refl} = \frac{[(\beta-1) - 2K\sqrt{\beta}]^2}{(\beta+1)^2} P_g$$

More Useful Equations

- For β large,

$$P_g \simeq \frac{1}{4R_L} (V_c + I_0 R_L)^2$$

$$P_{refl} \simeq \frac{1}{4R_L} (V_c - I_0 R_L)^2$$

- For $P_{refl}=0$ (condition for matching) \Rightarrow

$$R_L = \frac{V_c^M}{I_0^M}$$

and

$$P_g \simeq \frac{I_0^M V_c^M}{4} \left(\frac{V_c}{V_c^M} + \frac{I_0}{I_0^M} \right)^2$$

Example

- For $V_c=14$ MV, $L=0.7$ m, $Q_L=2 \times 10^7$, $Q_0=1 \times 10^{10}$:

Power	$I_0 = 0$	$I_0 = 100 \mu\text{A}$	$I_0 = 1 \text{ mA}$
P_g	3.65 kW	4.38 kW	14.033 kW
P_{diss}	29 W	29 W	29 W
$I_0 V_c$	0 W	1.4 kW	14 kW
P_{refl}	3.62 kW	2.951 kW	~ 4.4 W

Off Crest/Off Resonance Operation



- Typically electron storage rings operate off crest in order to ensure stability against phase oscillations.
- As a consequence, the rf cavities must be detuned off resonance in order to minimize the reflected power and the required generator power.
- Longitudinal gymnastics may also impose off crest operation in recirculating linacs.

- We write the beam current and the cavity voltage as

$$\tilde{I}_b = 2I_0 e^{i\psi_b}$$

$$\tilde{V}_c = V_c e^{i\psi_c} \quad \text{and set } \psi_c = 0$$

- The generator power can then be expressed as:

$$P_g = \frac{V_c^2}{R_L} \frac{(1+\beta)}{4\beta} \left\{ \left[1 + \frac{I_0 R_L}{V_c} \cos \psi_b \right]^2 + \left[\tan \Psi - \frac{I_0 R_L}{V_c} \sin \psi_b \right]^2 \right\}$$

Wiedemann
16.31

Off Crest/Off Resonance Operation



- Condition for optimum tuning:

$$\tan \Psi = \frac{I_0 R_L}{V_c} \sin \psi_b$$

- Condition for optimum coupling:

$$\beta_{\text{opt}} = 1 + \frac{I_0 R_a}{V_c} \cos \psi_b$$

- Minimum generator power:

$$P_{g,\text{min}} = \frac{V_c^2 \beta_{\text{opt}}}{R_a}$$

Wiedemann
16.36