

USPAS Course
on
Recirculated and Energy Recovered
Linear Accelerators

G. A. Krafft and L. Merminga

Jefferson Lab

and

Ivan Bazarov

Cornell University

Lecture 10



Outline

- Introduction
- Cavity Fundamental Parameters
- RF Cavity as a Parallel LCR Circuit
- Coupling of Cavity to an rf Generator
- Equivalent Circuit for a Cavity with Beam Loading
 - On Crest and on Resonance Operation
 - Off Crest and off Resonance Operation
 - ◆ Optimum Tuning
 - ◆ Optimum Coupling
- RF cavity with Beam and Microphonics
- Q_{ext} Optimization under Beam Loading and Microphonics
- RF Modeling
- Conclusions



Introduction

- Goal: Ability to predict rf cavity's steady-state response and develop a differential equation for the transient response
- We will construct an equivalent circuit and analyze it
- We will write the quantities that characterize an rf cavity and relate them to the circuit parameters, for
 - a) a cavity
 - b) a cavity coupled to an rf generator
 - c) a cavity with beam



RF Cavity Fundamental Quantities

- Quality Factor Q_0 :

$$Q_0 \equiv \frac{\omega_0 W}{P_{diss}} = \frac{\text{Energy stored in cavity}}{\text{Energy dissipated in cavity walls per radian}}$$

- Shunt impedance R_a :

$$R_a \equiv \frac{V_a^2}{P_{diss}} \quad \text{in ohms per cell}$$

(accelerator definition); V_a = accelerating voltage

- Note: Voltages and currents will be represented as complex quantities, denoted by a tilde. For example:


$$V_c(t) = \text{Re} \left\{ \tilde{V}_c(t) e^{i\omega t} \right\} \quad \tilde{V}_c(t) = V_c e^{i\phi(t)}$$

where $V_c = |\tilde{V}_c|$ is the magnitude of \tilde{V}_c and ϕ is a slowly varying phase.




Equivalent Circuit for an rf Cavity

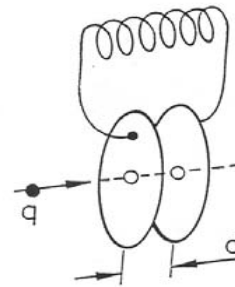Simple LC circuit representing an accelerating resonator.



Simple lumped L-C circuit representing an accelerating resonator.
 $\omega_0^2 = 1/LC$

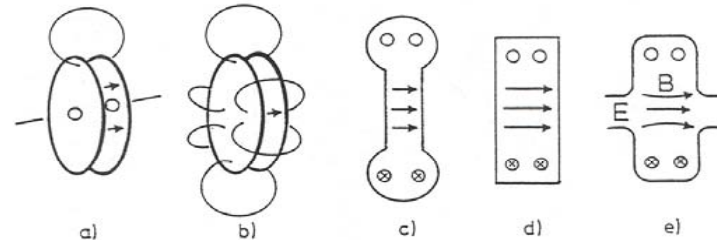
Metamorphosis of the LC circuit into an accelerating cavity.




Metamorphosis of the L-C circuit of Fig. 1 into an accelerating cavity (after R.P.Feynman³³). Fig. 5d shows the cylindrical "pillbox cavity" and Fig. 5e a slightly modified pillbox cavity with beam holes (typical β between 0.5 and 1.0). Fig. 5c resembles a low β version of the pillbox variety ($0.2 < \beta < 0.5$).

Chain of weakly coupled pillbox cavities representing an accelerating cavity.

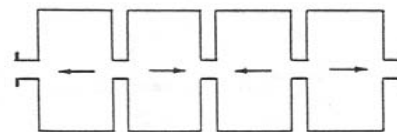Chain of coupled pendula as its mechanical analogue.



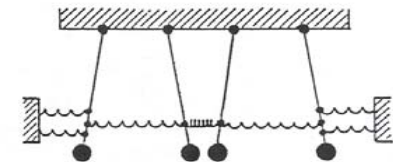Chain of weakly-coupled pillbox cavities representing an accelerating module




Chain of coupled pendula as a mechanical analogue to Fig. 6a



Equivalent Circuit for an rf Cavity (cont'd)

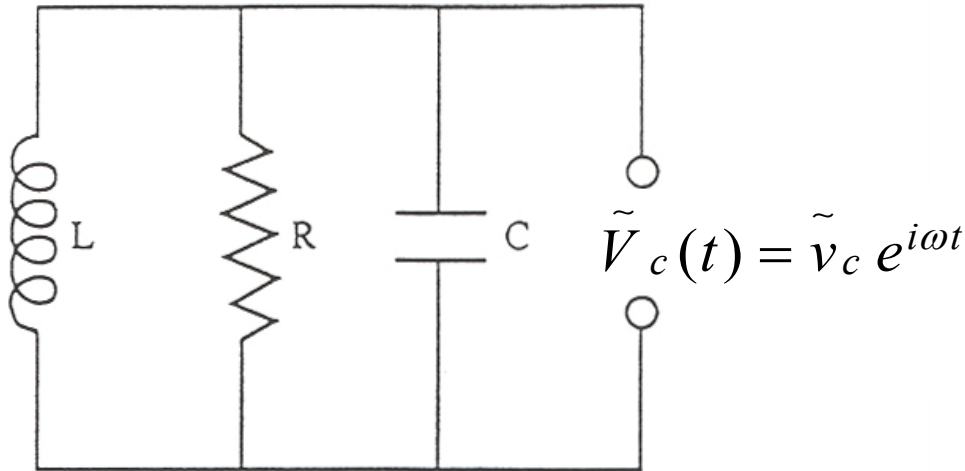- An rf cavity can be represented by a parallel LCR circuit:



- Impedance Z of the equivalent circuit:
$$\tilde{Z} = \left[\frac{1}{R} + \frac{1}{iL\omega} + iC\omega \right]^{-1}$$
- Resonant frequency of the circuit:
$$\omega_0 = 1/\sqrt{LC}$$
- Stored energy W :
$$W = \frac{1}{2} C V_c^2$$



Equivalent Circuit for an rf Cavity (cont'd)

■ Power dissipated in resistor R :
$$P_{diss} = \frac{1}{2} \frac{V_c^2}{R}$$

■ From definition of shunt impedance $R_a \equiv \frac{V_a^2}{P_{diss}} \quad \therefore R_a = 2R$


■ Quality factor of resonator:
$$Q_0 \equiv \frac{\omega_0 W}{P_{diss}} = \omega_0 CR$$

■ Note:
$$\tilde{Z} = R \left[1 + iQ_0 \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right) \right]^{-1} \quad \text{For } \omega \approx \omega_0, \quad \tilde{Z} \approx R \left[1 + 2iQ_0 \left(\frac{\omega - \omega_0}{\omega_0} \right) \right]^{-1}$$



Cavity with External Coupling

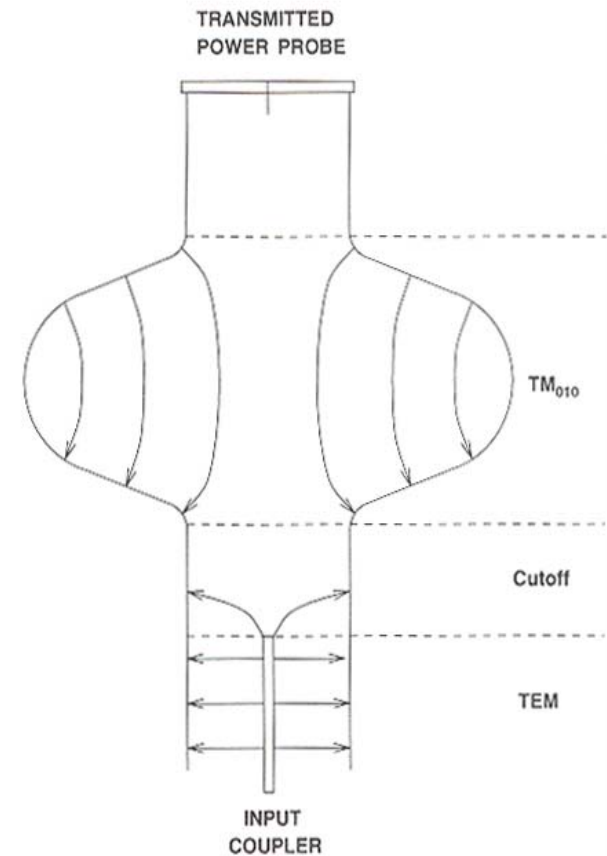- Consider a cavity connected to an rf source
- A coaxial cable carries power from an rf source to the cavity
- The strength of the input coupler is adjusted by changing the penetration of the center conductor
- There is a fixed output coupler, the *transmitted power probe*, which picks up power transmitted through the cavity



Cavity with External Coupling (cont'd)

Consider the rf cavity after the rf is turned off.

Stored energy W satisfies the equation:

$$\frac{dW}{dt} = -P_{tot}$$

Total power being lost, P_{tot} , is: $P_{tot} = P_{diss} + P_e + P_t$

P_e is the power leaking back out the input coupler. P_t is the power coming out the transmitted power coupler. Typically P_t is very small $\Rightarrow P_{tot} \approx P_{diss} + P_e$

Recall $Q_0 \equiv \frac{\omega_0 W}{P_{diss}}$

Similarly define a “loaded” quality factor Q_L : $Q_L \equiv \frac{\omega_0 W}{P_{tot}}$

Now $\frac{dW}{dt} = -\frac{\omega_0 W}{Q_L} \Rightarrow W = W_0 e^{-\frac{\omega_0 t}{Q_L}}$

\therefore energy in the cavity decays exponentially with time constant: $\tau_L = \frac{Q_L}{\omega_0}$



Cavity with External Coupling (cont'd)

Equation

$$\frac{P_{tot}}{\omega_0 W} = \frac{P_{diss} + P_e}{\omega_0 W}$$

suggests that we can assign a quality factor to each loss mechanism, such that

$$\frac{1}{Q_L} = \frac{1}{Q_0} + \frac{1}{Q_e}$$

where, by definition,

$$Q_e \equiv \frac{\omega_0 W}{P_e}$$

Typical values for CEBAF 7-cell cavities: $Q_0 = 1 \times 10^{10}$, $Q_e \approx Q_L = 2 \times 10^7$.



Cavity with External Coupling (cont'd)

- Define “coupling parameter”:

$$\beta \equiv \frac{Q_0}{Q_e}$$

therefore

$$\frac{1}{Q_L} = \frac{(1 + \beta)}{Q_0}$$

- β is equal to:


$$\beta = \frac{P_e}{P_{diss}}$$

It tells us how strongly the couplers interact with the cavity. Large β implies that the power leaking out of the coupler is large compared to the power dissipated in the cavity walls.




Equivalent Circuit of a Cavity Coupled to an rf Source

- The system we want to model:

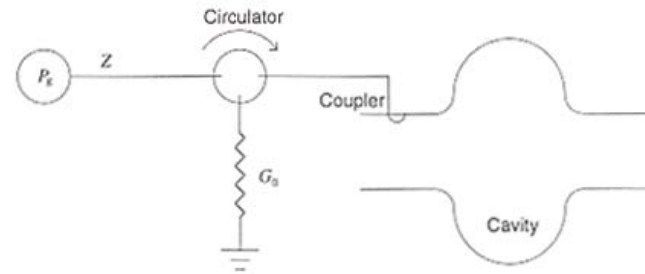

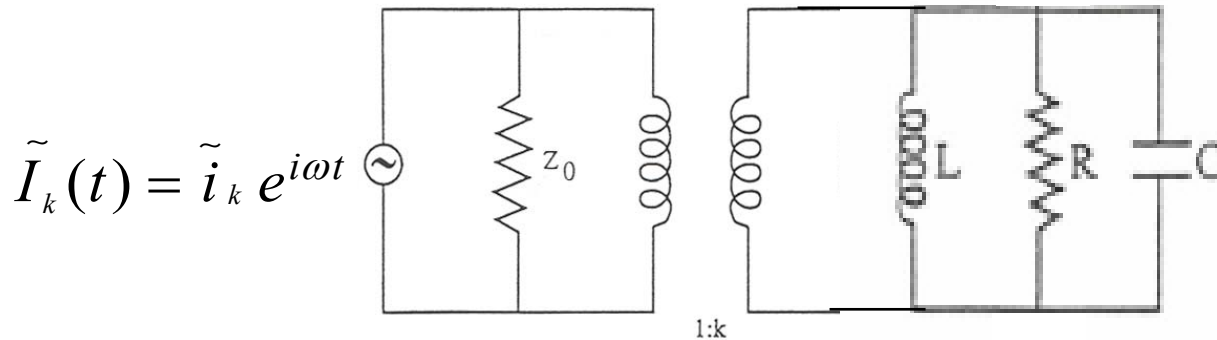- Between the rf generator and the cavity is an isolator – a circulator connected to a load. Circulator ensures that signals coming from the cavity are terminated in a matched load.
- Equivalent circuit:





RF Generator + Circulator Coupler

Cavity

- Coupling is represented by an ideal transformer of turn ratio 1:k



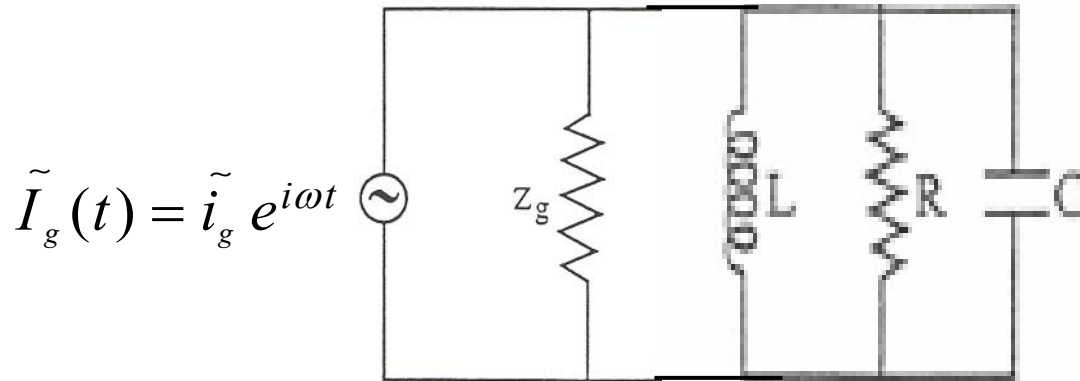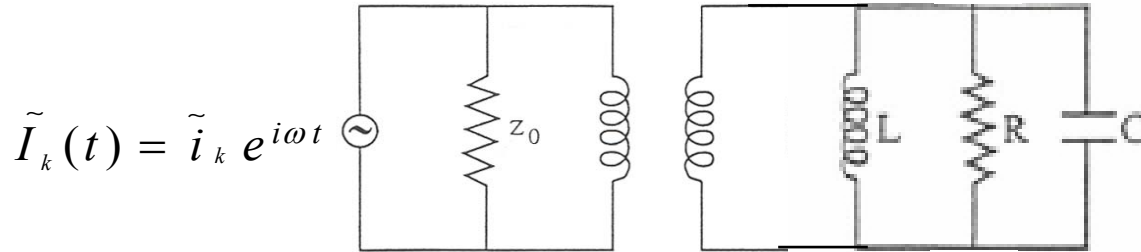Equivalent Circuit of a Cavity Coupled to an rf Source



$$I_g = \frac{I_k}{k}$$

$$Z_g = k^2 Z_0$$


By definition,

$$\beta \equiv \frac{R}{Z_g} = \frac{R}{k^2 Z_0} \quad \therefore \quad Z_g = \frac{R}{\beta}$$



Generator Power

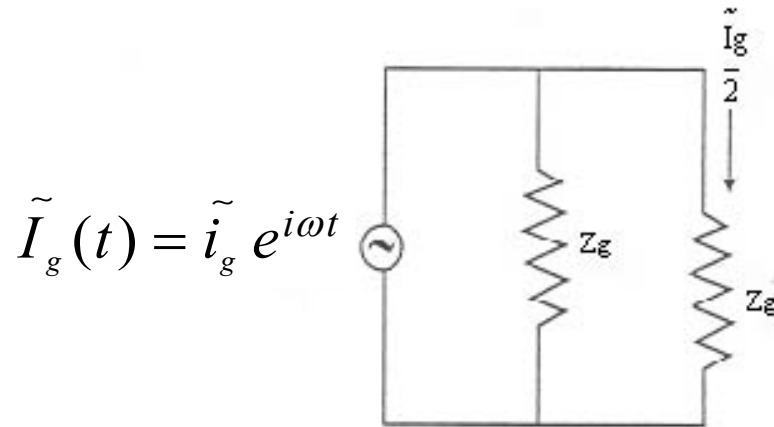- When the cavity is matched to the input circuit, the power dissipation in the cavity is maximized.



$$P_{diss}^{\max} = \frac{1}{2} Z_g \left(\frac{I_g}{2} \right)^2 \quad \text{or} \quad P_{diss}^{\max} = \frac{1}{16\beta} R_a I_g^2 \equiv P_g$$

- We define the available generator power P_g at a given generator current \tilde{I}_g to be equal to P_{diss}^{\max} .



Some Useful Expressions

- We derive expressions for W , P_{diss} , P_{refl} , in terms of cavity parameters

$$\frac{W}{P_g} = \frac{\frac{Q_0}{\omega_0} P_{diss}}{\frac{1}{16\beta} R_a I_g^2} = \frac{\frac{Q_0}{\omega_0} \frac{V_c^2}{R_a}}{\frac{1}{16\beta} R_a I_g^2} = \frac{16\beta}{R_a^2} \frac{Q_0}{\omega_0} \frac{V_c^2}{I_g^2}$$

$$V_c = I_g Z_{TOT}$$

$$Z_{TOT} = \left[\frac{1}{Z_g} + \frac{1}{Z} \right]^{-1}$$

$$Z_{TOT} = \frac{R_a}{2} \left[(1 + \beta) + iQ_0 \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right) \right]^{-1}$$

$$\therefore W = 4\beta \frac{Q_0}{\omega_0} \frac{1}{(1 + \beta)^2 + Q_0^2 \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right)^2} P_g$$

For $\omega \approx \omega_0 \Rightarrow$

$$W \approx \frac{4\beta}{(1 + \beta)^2} \frac{Q_0}{\omega_0} \frac{1}{1 + \left[2 \frac{Q_0}{(1 + \beta)} \frac{\omega - \omega_0}{\omega_0} \right]^2} P_g$$



Some Useful Expressions (cont'd)

$$W \approx \frac{4\beta}{(1+\beta)^2} \frac{Q_0}{\omega_0} \frac{1}{1 + \left[2 \frac{Q_0}{(1+\beta)} \frac{\omega - \omega_0}{\omega_0} \right]^2} P_g$$

- Define “Tuning angle” Ψ :

$$\tan \Psi \equiv -Q_L \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right) \approx -2Q_L \frac{\omega - \omega_0}{\omega_0} \quad \text{for } \omega \approx \omega_0$$

\therefore

$$W = \frac{4\beta}{(1+\beta)^2} \frac{Q_0}{\omega_0} \frac{1}{1 + \tan^2 \Psi} P_g$$

- Recall:

$$P_{diss} = \frac{\omega_0 W}{Q_0}$$

\therefore

$$P_{diss} = \frac{4\beta}{(1+\beta)^2} \frac{1}{1 + \tan^2 \Psi} P_g$$



Some Useful Expressions (cont'd)

- Optimal coupling: W/P_g maximum or $P_{diss} = P_g$
which implies $\Delta\omega = 0$, $\beta = 1$
this is the case of critical coupling

- Reflected power is calculated from energy conservation:


$$P_{refl} = P_g - P_{diss}$$

$$P_{refl} = P_g \left[1 - \frac{4\beta}{(1+\beta)^2} \frac{1}{1 + \tan^2 \Psi} \right]$$

- On resonance: $W = \frac{4\beta}{(1+\beta)^2} \frac{Q_0}{\omega_0} P_g$


$$P_{diss} = \frac{4\beta}{(1+\beta)^2} P_g$$
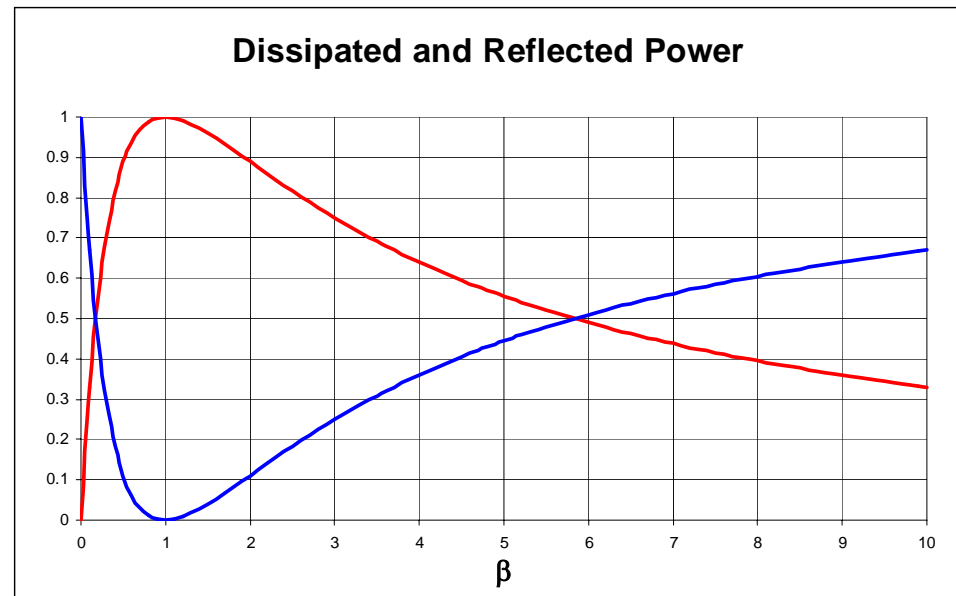
$$P_{refl} = \left(\frac{1-\beta}{1+\beta} \right)^2 P_g$$



Equivalent Circuit for a Cavity with Beam

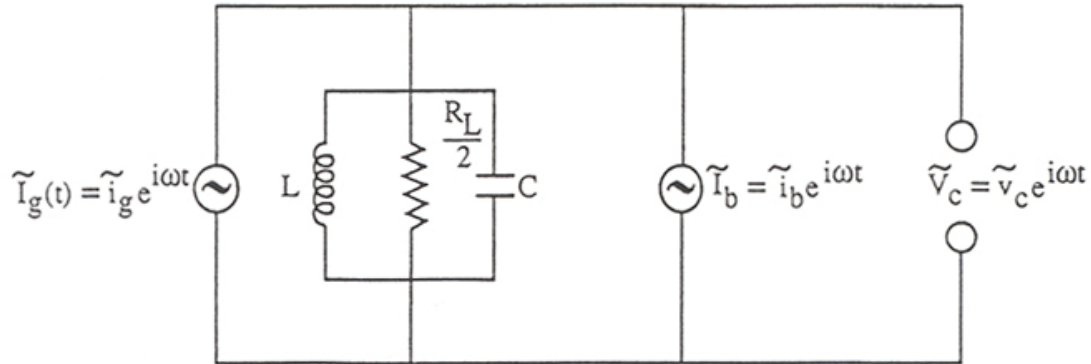- Beam in the rf cavity is represented by a current generator.
- Equivalent circuit:



- Differential equation that describes the dynamics of the system:

$$i_C = C \frac{dv_C}{dt}, \quad i_R = \frac{v_C}{R_L/2}, \quad v_C = L \frac{di_L}{dt}$$

- R_L is the loaded impedance defined as: $R_L = \frac{R_a}{(1 + \beta)}$



Equivalent Circuit for a Cavity with Beam (cont'd)

- Kirchoff's law:
$$\tilde{i}_L + \tilde{i}_R + \tilde{i}_C = \tilde{i}_g - \tilde{i}_b$$
- Total current is a superposition of generator current and beam current and beam current opposes the generator current.

$$\frac{d^2 \tilde{v}_c}{dt^2} + \frac{\omega_0}{Q_L} \frac{d\tilde{v}_c}{dt} + \omega_0^2 \tilde{v}_c = \frac{\omega_0 R_L}{2Q_L} \frac{d}{dt} (\tilde{i}_g - \tilde{i}_b)$$

- Assume that $\tilde{v}_c, \tilde{i}_g, \tilde{i}_b$ have a fast (rf) time-varying component and a slow varying component:

$$\tilde{v}_c = \tilde{V}_c e^{i\omega t}$$

$$\tilde{i}_g = \tilde{I}_g e^{i\omega t}$$

$$\tilde{i}_b = \tilde{I}_b e^{i\omega t}$$

where ω is the generator angular frequency and $\tilde{V}_c, \tilde{I}_g, \tilde{I}_b$ are complex quantities.



Equivalent Circuit for a Cavity with Beam (cont'd)

- Neglecting terms of order $\frac{d^2\tilde{V}_c}{dt^2}$, $\frac{d\tilde{I}}{dt}$, $\frac{1}{Q_L} \frac{d\tilde{V}_c}{dt}$ we arrive at:

$$\frac{d\tilde{V}_c}{dt} + \frac{\omega_0}{2Q_L} (1 - i \tan \Psi) \tilde{V}_c = \frac{\omega_0 R_L}{4Q_L} (\tilde{I}_g - \tilde{I}_b)$$

where Ψ is the tuning angle.

- For short bunches: $|\tilde{I}_b| \approx 2I_0$ where I_0 is the average beam current.



Equivalent Circuit for a Cavity with Beam (cont'd)

$$\frac{d\tilde{V}_c}{dt} + \frac{\omega_0}{2Q_L}(1 - i \tan \Psi)\tilde{V}_c = \frac{\omega_0 R_L}{4Q_L}(\tilde{I}_g - \tilde{I}_b)$$

■ At steady-state:

$$\tilde{V}_c = \frac{R_L/2}{(1 - i \tan \Psi)} \tilde{I}_g - \frac{R_L/2}{(1 - i \tan \Psi)} \tilde{I}_b$$

or

$$\tilde{V}_c = \frac{R_L}{2} \tilde{I}_g \cos \Psi e^{i\Psi} - \frac{R_L}{2} \tilde{I}_b \cos \Psi e^{i\Psi}$$

or

$$\tilde{V}_c = \boxed{\tilde{V}_{gr} \cos \Psi e^{i\Psi}} + \boxed{\tilde{V}_{br} \cos \Psi e^{i\Psi}}$$

or

$$\tilde{V}_c = \tilde{V}_g + \tilde{V}_b$$

$$\left\{ \begin{array}{l} \tilde{V}_{gr} = \frac{R_L}{2} \tilde{I}_g \\ \tilde{V}_{br} = -\frac{R_L}{2} \tilde{I}_b \end{array} \right\}$$

are the generator and beam-loading voltages on resonance

and $\left\{ \begin{array}{l} \tilde{V}_g \\ \tilde{V}_b \end{array} \right\}$ are the generator and beam-loading voltages.



Equivalent Circuit for a Cavity with Beam (cont'd)


- Note that:

$$|\tilde{V}_{gr}| = \frac{2\sqrt{\beta}}{\sqrt{1+\beta}} \sqrt{P_g R_L} \approx 2\sqrt{P_g R_L} \quad \text{for large } \beta$$

$$|\tilde{V}_{br}| = R_L I_0$$



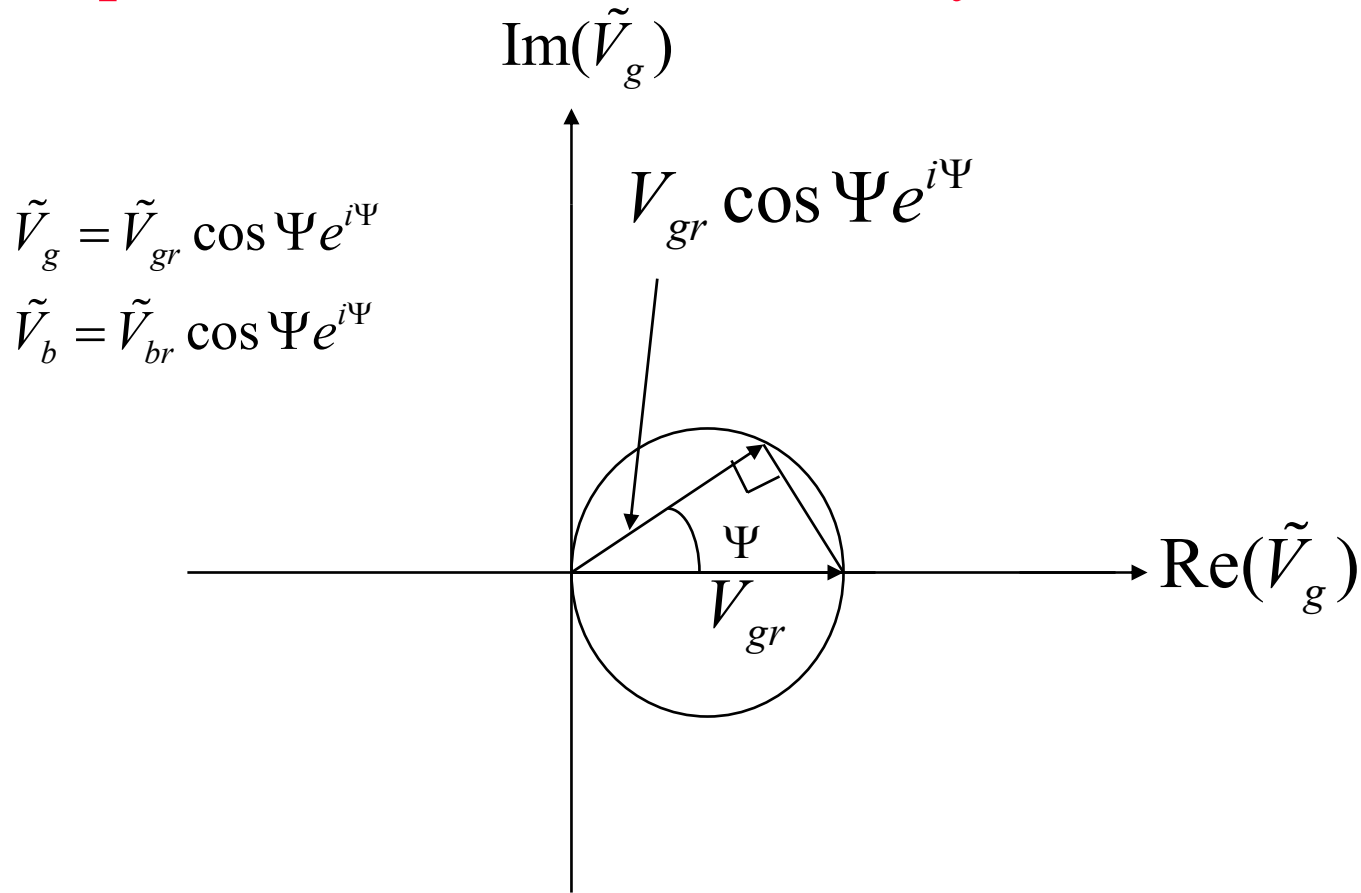Equivalent Circuit for a Cavity with Beam (cont'd)



As Ψ increases the magnitude of both V_g and V_b decreases while their phases rotate by Ψ .




Equivalent Circuit for a Cavity with Beam (cont'd)

$$\tilde{V}_c = \tilde{V}_g + \tilde{V}_b$$

- Cavity voltage is the superposition of the generator and beam-loading voltage.
- This is the basis for the vector diagram analysis.




Example of a Phasor Diagram

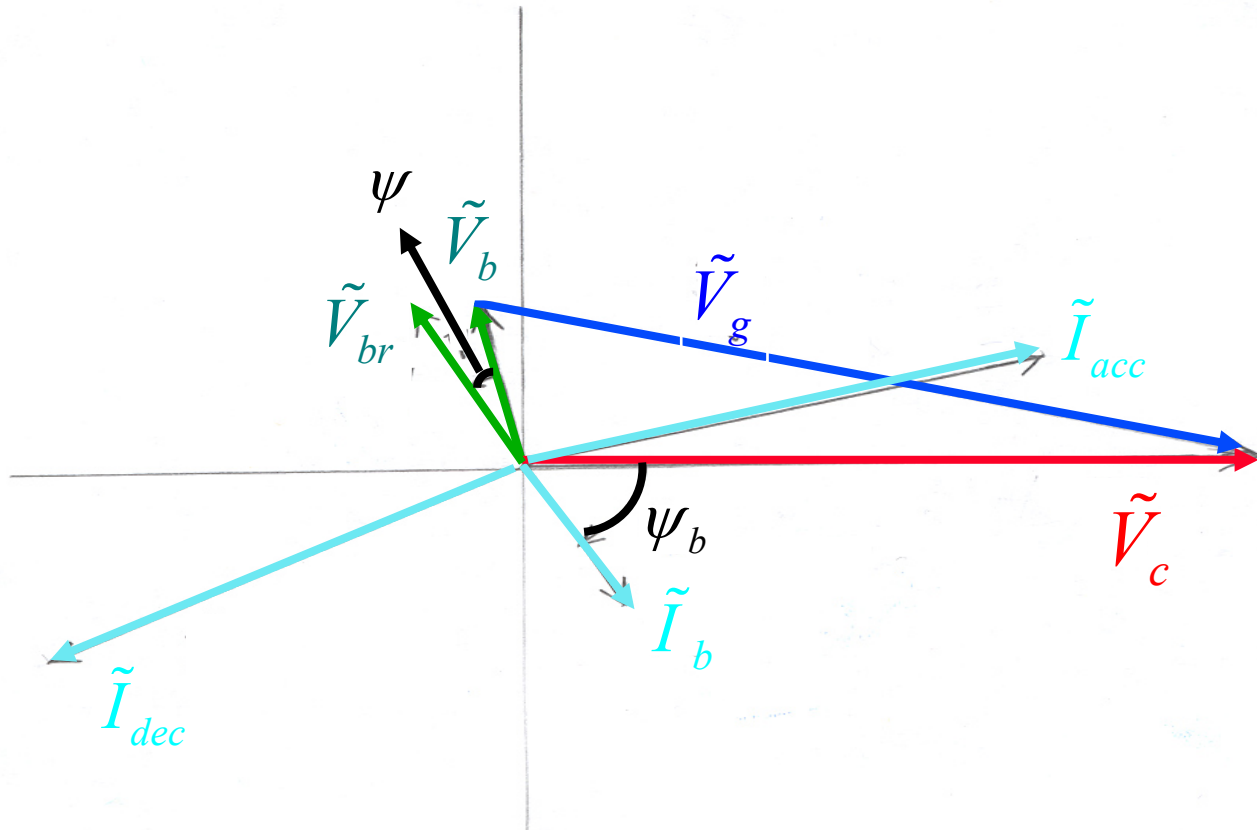

On Crest and On Resonance Operation

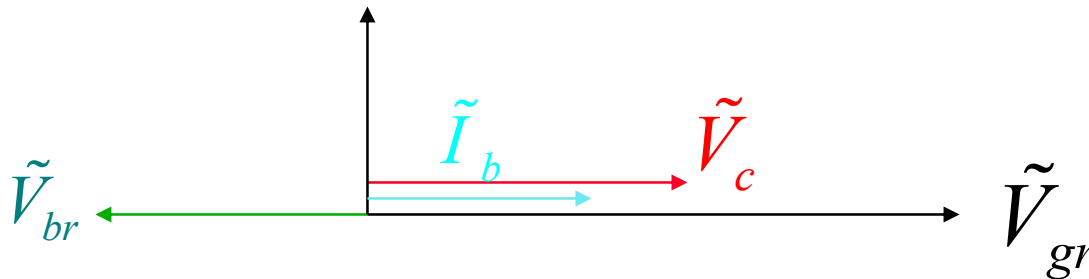- Typically linacs operate on resonance and on crest in order to receive maximum acceleration.
- On crest and on resonance



$$\Rightarrow V_a = V_{gr} - V_{br}$$

where V_a is the accelerating voltage.



More Useful Equations


- We derive expressions for W , V_a , P_{diss} , P_{refl} in terms of β and the loading parameter K , defined by: $K = I_0/2 \sqrt{R_a/P_g}$

From:

$$|\tilde{V}_{gr}| = \frac{2\sqrt{\beta}}{\sqrt{1+\beta}} \sqrt{P_g R_L}$$

$$|\tilde{V}_{br}| = R_L I_0$$

$$V_a = V_{gr} - V_{br}$$

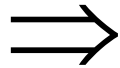

$$V_a = \sqrt{P_g R_a} \left\{ \frac{2\sqrt{\beta}}{\sqrt{1+\beta}} \left(1 - \frac{K}{\sqrt{\beta}} \right) \right\}$$

$$W = \frac{4\beta}{(1+\beta)^2} \frac{Q_0}{\omega_0} \left(1 - \frac{K}{\sqrt{\beta}} \right)^2 P_g$$

$$P_{diss} = \frac{4\beta}{(1+\beta)^2} \left(1 - \frac{K}{\sqrt{\beta}} \right)^2 P_g$$

$$I_0 V_a = I_0 \sqrt{R_a P_{diss}}$$

$$\eta \equiv \frac{I_0 V_a}{P_g} = \frac{2\sqrt{\beta}}{\sqrt{1+\beta}} 2K \left(1 - \frac{K}{\sqrt{\beta}} \right)$$

$$P_{refl} = P_g - P_{diss} - I_0 V_a \Rightarrow P_{refl} = \frac{\left[(\beta - 1) - 2K\sqrt{\beta} \right]^2}{(\beta + 1)^2} P_g$$



More Useful Equations (cont'd)

- For β large,

$$P_g \simeq \frac{1}{4R_L}(V_a + I_0 R_L)^2$$

$$P_{refl} \simeq \frac{1}{4R_L}(V_a - I_0 R_L)^2$$

- For $P_{refl}=0$ (condition for matching) \Rightarrow

$$R_L = \frac{V_a^M}{I_0^M}$$

and

$$P_g \simeq \frac{I_0^M V_a^M}{4} \left(\frac{V_a}{V_a^M} + \frac{I_0}{I_0^M} \right)^2$$



Example

- For $V_a=20$ MV/m, $L=0.7$ m, $Q_L=2 \times 10^7$, $Q_0=1 \times 10^{10}$:

Power	$I_0 = 0$	$I_0 = 100 \mu\text{A}$	$I_0 = 1 \text{ mA}$
P_g	3.65 kW	4.38 kW	14.033 kW
P_{diss}	29 W	29 W	29 W
$I_0 V_a$	0 W	1.4 kW	14 kW
P_{refl}	3.62 kW	2.951 kW	~ 4.4 W



Off Crest and Off Resonance Operation

- Typically electron storage rings operate off crest in order to ensure stability against phase oscillations.
- As a consequence, the rf cavities must be detuned off resonance in order to minimize the reflected power and the required generator power.
- Longitudinal gymnastics may also impose off crest operation in recirculating linacs.
- We write the beam current and the cavity voltage as

$$\tilde{I}_b = 2I_0 e^{i\psi_b}$$

$$\tilde{V}_c = V_c e^{i\psi_c} \quad \text{and set } \psi_c = 0$$

- The generator power can then be expressed as:

$$P_g = \frac{V_c^2 (1 + \beta)}{R_L 4\beta} \left\{ \left[1 + \frac{I_0 R_L}{V_c} \cos \psi_b \right]^2 + \left[\tan \Psi - \frac{I_0 R_L}{V_c} \sin \psi_b \right]^2 \right\}$$



Off Crest and Off Resonance Operation (cont'd)

- Condition for optimum tuning:

$$\tan \Psi = \frac{I_0 R_L}{V_c} \sin \psi_b$$

- Condition for optimum coupling:

$$\beta_0 = 1 + \frac{I_0 R_a}{V_c} \cos \psi_b$$

- Minimum generator power:

$$P_{g,\min} = \frac{V_c^2 \beta_0}{R_a}$$





RF Cavity with Beam and Microphonics

The detuning is now: $\tan \Psi = -2Q_L \frac{\delta f_0 \pm \delta f_m}{f_0}$ $\tan \psi_0 = -2Q_L \frac{\delta f_0}{f_0}$

where δf_0 is the static detuning (controllable)

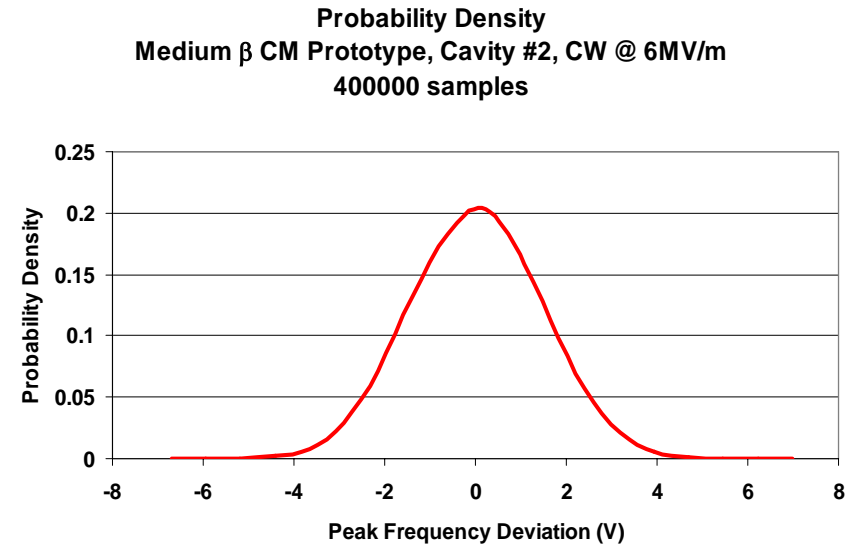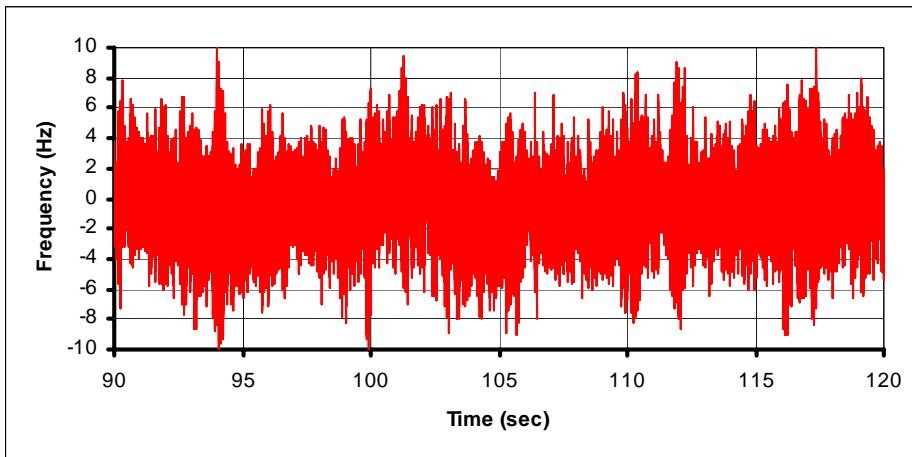and δf_m is the random dynamic detuning (uncontrollable)



Q_{ext} Optimization under Beam Loading and Microphonics

- Beam loading and microphonics require careful optimization of the external Q of cavities.
- Derive expressions for the optimum setting of cavity parameters when operating under
 - a) heavy beam loading
 - b) little or no beam loading, as is the case in energy recovery linac cavities and in the presence of microphonics.



Q_{ext} Optimization (cont'd)

$$P_g = \frac{V_c^2}{R_L} \frac{(1 + \beta)}{4\beta} \left\{ \left[1 + \frac{I_{\text{tot}} R_L}{V_c} \cos \psi_{\text{tot}} \right]^2 + \left[\tan \Psi - \frac{I_{\text{tot}} R_L}{V_c} \sin \psi_{\text{tot}} \right]^2 \right\}$$

$$\tan \Psi = -2Q_L \frac{\delta f}{f_0}$$

where δf is the total amount of cavity detuning in Hz, including static detuning and microphonics.

- Optimization of the generator power with respect to coupling gives:

$$\beta_{\text{opt}} = \sqrt{(b + 1)^2 + \left[2Q_0 \frac{\delta f}{f_0} + b \tan \psi_{\text{tot}} \right]^2}$$

where $b \equiv \frac{I_{\text{tot}} R_a}{V_c} \cos \psi_{\text{tot}}$

where I_{tot} is the magnitude of the resultant beam current vector in the cavity and ψ_{tot} is the phase of the resultant beam vector with respect to the cavity voltage.



Q_{ext} Optimization (cont'd)

$$P_g = \frac{V_c^2 (1 + \beta)}{R_L 4\beta} \left\{ \left[1 + \frac{I_{\text{tot}} R_L}{V_c} \cos \psi_{\text{tot}} \right]^2 + \left[\tan \Psi - \frac{I_{\text{tot}} R_L}{V_c} \sin \psi_{\text{tot}} \right]^2 \right\}$$

where: $\tan \Psi = -2Q_L \frac{\delta f_0 + \delta f_m}{f_0}$

- To minimize generator power with respect to tuning:

$$\delta f_0 = -\frac{f_0}{2Q_0} b \tan \Psi$$

\Rightarrow

$$P_g = \frac{V_c^2 (1 + \beta)}{R_L 4\beta} \left\{ (1 + b + \beta)^2 + \left[2Q_0 \frac{\delta f_m}{f_0} \right]^2 \right\}$$



Q_{ext} Optimization (cont'd)

- Condition for optimum coupling:

$$\beta_{\text{opt}} = \sqrt{(b+1)^2 + \left(2Q_0 \frac{\delta f_m}{f_0}\right)^2}$$

and

$$P_g^{\text{opt}} = \frac{V_c^2}{2R_a} \left[b+1 + \sqrt{(b+1)^2 + \left(2Q_0 \frac{\delta f_m}{f_0}\right)^2} \right]$$

- In the absence of beam ($b=0$):

$$\beta_{\text{opt}} = \sqrt{1 + \left(2Q_0 \frac{\delta f_m}{f_0}\right)^2}$$

and

$$P_g^{\text{opt}} = \frac{V_c^2}{2R_a} \left[1 + \sqrt{1 + \left(2Q_0 \frac{\delta f_m}{f_0}\right)^2} \right]$$



Homework

- Assuming no microphonics, plot β_{opt} and P_{opt}^g as function of b (beam loading), $b=-5$ to 5 , and explain the results.
- How do the results change if microphonics is present?



Example

- ERL Injector and Linac:

$\delta f_m = 25$ Hz, $Q_0 = 1 \times 10^{10}$, $f_0 = 1300$ MHz, $I_0 = 100$ mA, $V_c = 20$ MV/m, $L = 1.04$ m,
 $R_a/Q_0 = 1036$ ohms per cavity

- ERL linac: Resultant beam current, $I_{\text{tot}} = 0$ mA (energy recovery)

and $\beta_{\text{opt}} = 385 \Rightarrow Q_L = 2.6 \times 10^7 \Rightarrow P_g = 4$ kW per cavity.

- ERL Injector: $I_0 = 100$ mA and $\beta_{\text{opt}} = 5 \times 10^4 ! \Rightarrow Q_L = 2 \times 10^5 \Rightarrow P_g = 2.08$ MW per cavity!

Note: $I_0 V_a = 2.08$ MW \Rightarrow optimization is entirely dominated by beam loading.




RF System Modeling



- To include amplitude and phase feedback, nonlinear effects from the klystron and be able to analyze transient response of the system, response to large parameter variations or beam current fluctuations
 - we developed a model of the cavity and low level controls using SIMULINK, a MATLAB-based program for simulating dynamic systems.
- Model describes the beam-cavity interaction, includes a realistic representation of low level controls, klystron characteristics, microphonic noise, Lorentz force detuning and coupling and excitation of mechanical resonances



RF System Model

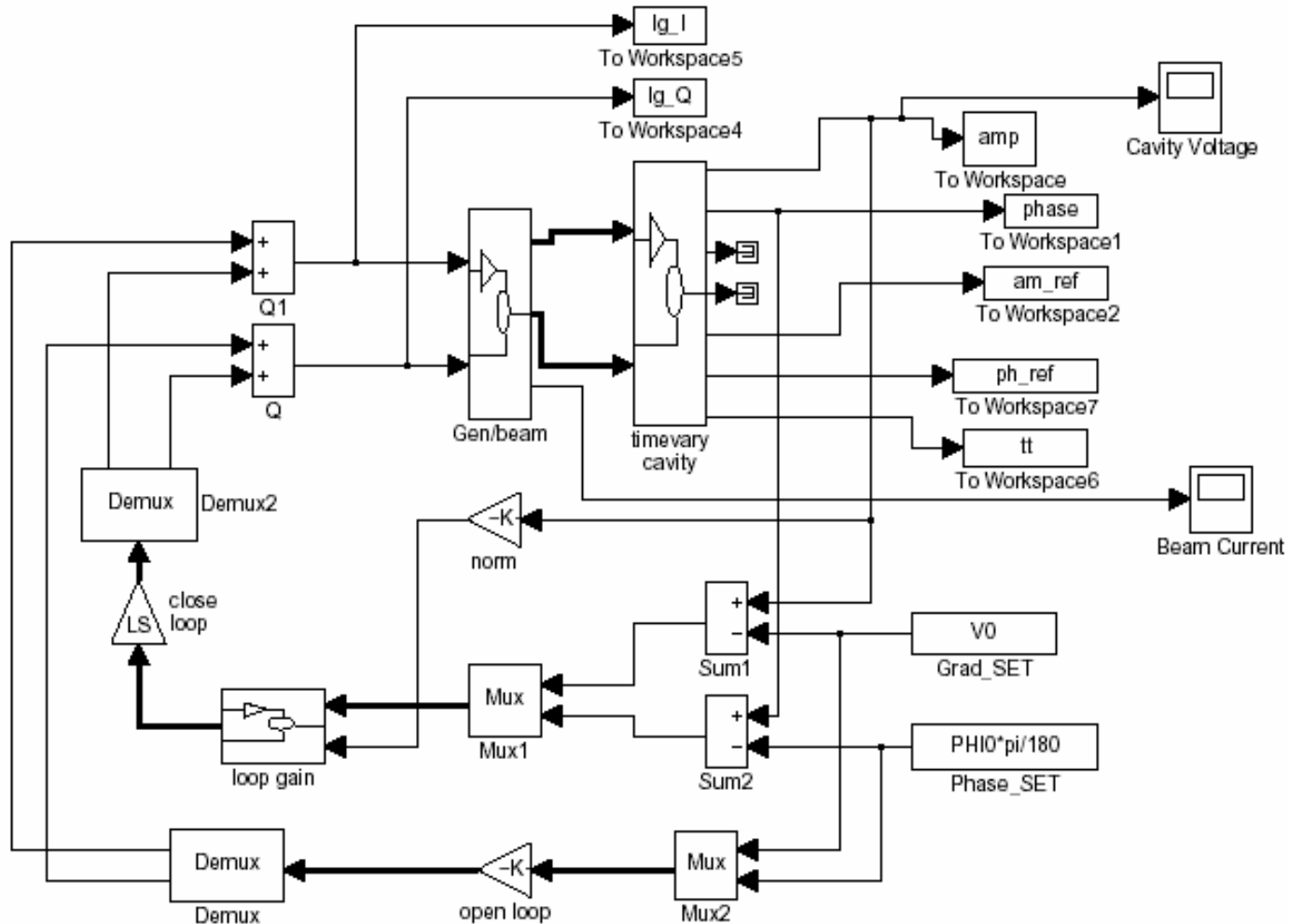

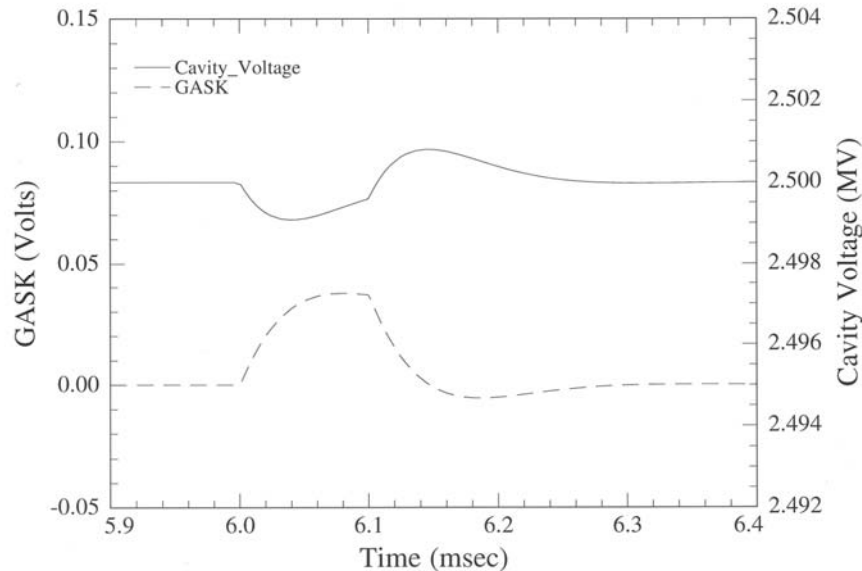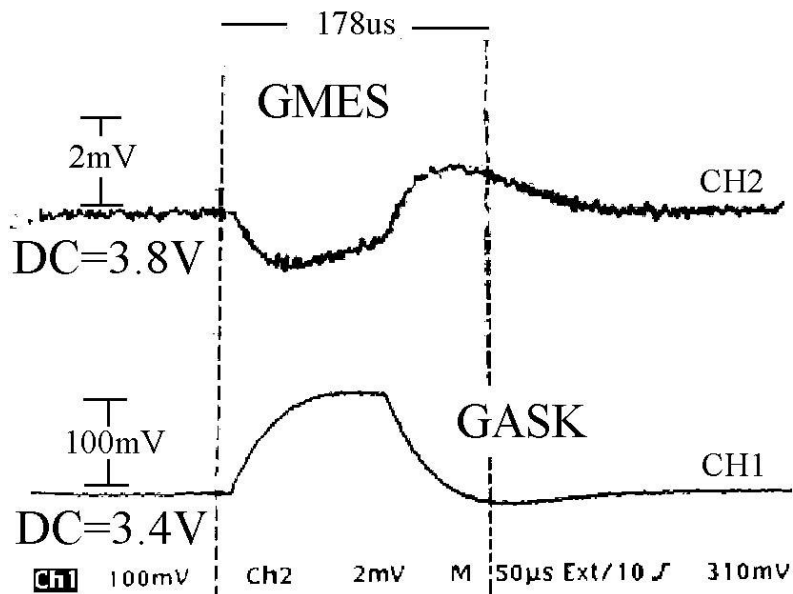RF Modeling: Simulations vs. Experimental Data



Measured and simulated cavity voltage and amplified gradient error signal (GASK) in one of CEBAF's cavities, when a 65 μ A, 100 μ sec beam pulse enters the cavity.



Conclusions

- We derived a differential equation that describes to a very good approximation the rf cavity and its interaction with beam.
- We derived useful relations among cavity's parameters and used phasor diagrams to analyze steady-state situations.
- We presented formula for the optimization of Q_{ext} under beam loading and microphonics.
- We showed an example of a Simulink model of the rf control system which can be useful when nonlinearities can not be ignored.

